

(For undergraduates: 2 lowest (wrong) questions will be dropped.)

Each question is 3 points, unless specified otherwise.

Name Sabina Mentukh

Section: Practice CpE 151 EEE 234

1. P-type semiconductor has electrons (electrons/holes) as minority charge carriers.
2. When a voltage of 2V is applied between the G and S of a NMOS, the transistor is: (assume  $V_t = 1\text{ V}$ )  
☒ (a) ON      (b) OFF      (c) Not enough information
3. When a voltage of -2V is applied to between the G and S of a PMOS transistor, the transistor is (Assume  $|V_{tp}| = 1\text{ V}$ ):  
☒ (a) ON      (b) OFF      (c) Not enough information
4. Pick the most appropriate statement from below. A 3-input NOR gate has:  
(a) 3 NMOS transistors in the Pull Down Network  
(b) 3 PMOS transistors in the Pull Down Network  
(c) 3 NMOS transistors in parallel and 3 PMOS transistors in series  
(d) 3 NMOS transistors in series and 3 PMOS transistors in parallel  
☒ (e) Both (a) and (c) are true  
(f) Both (b) and (d) are true
5. If the NMOS and PMOS transistors switch places in an inverter, the resulting circuit is:  
(a) Weak Inverter  
(b) Strong Inverter  
☒ (c) Weak buffer  
(d) Strong buffer
6. Which of the following is true about PMOS transistor?  
☒ (a) It provides a good '1'  
(b) It provides a good '0'  
(c) It uses p-well  
(d) It has positive threshold voltage  $V_{tp}$
7. Input dependent phase shift is brought about by which of the following transistor non-ideality?  
a. Channel-charge injection  
b. Clock-feed through  
☒ c. Non-zero ON-resistance  
d. Negative-bias Temperature Instability (NBTI)

8. A 2:1 MUX implemented using transmission gates has uses how many PMOS transistors?

2

9. Which of the following Capacitances is fundamental to the operation of a MOS transistor?

- a. Depletion capacitance between Drain and Bulk
- b. Depletion capacitance between Source and Bulk
- c. Overlap Capacitance between Gate and Source Drain
- ☒ d. Oxide Capacitance between Gate and Channel

10. In the Figure – 1 shown below, which capacitance shorts the input to the output at high frequencies?

 


Figure – 1. MOSFET Capacitances

11. In the Figure – 2 shown below, plot the graph for the equivalent ON-resistance of a transmission gate. The On-resistance of NMOS and PMOS as a function of  $V_{in}$ .

 


Figure – 2. On-resistance of NMOS, PMOS and transmission gate

12. Shown below are transistor higher order effects. Identify a lateral field effect from below.

- a. Subthreshold conduction
- ☒ b. Mobility degradation
- c. Body effect
- ☒ d. Velocity saturation

13. Shown below are transistor higher order effects. Identify a vertical field effect from below.

- a. Subthreshold conduction
- ☒ b. Mobility degradation
- c. Body effect
- d. Velocity saturation

14. "Pinch-off" occurs in which region of operation?

- a. Subthreshold
- ☒ b. Saturation
- c. Linear
- d. Both (b) and (c)

15. Because of short channel effect, the  $V_{TH}$  of a MOSFET increases (increases/decreases) with increasing values of  $L$ .

16. For the pass transistor shown in figure - 3 below, what is the voltage at the output?

 


Figure - 3 PMOS Pass Transistor

17. By definition, the time from input to rising output crossing  $V_{DD}/2$  is:

- a. Rise Time - ( $t_r$ )
- ☒ b. Rising Propagation Delay ( $t_{pdr}$ )
- c. Rising Contamination delay ( $t_{cdr}$ )
- d. Setup - time

18. In RC Delay Model, which of the following substitutions is valid

- a. PMOS transistor with a width of  $k$  times the unit transistor has a resistance of  $R/k$
- b. NMOS transistor with a width of  $k$  times the unit transistor has a cap of  $2kC$  on the gate
- ☒ c. PMOS transistor with a width of  $k$  times the unit transistor has a cap of  $kC$  on the gate
- d. NMOS transistor with a width of  $k$  times the unit transistor has a resistance of  $2R/k$

19. While calculating the delay of a RC ladder using Elmore - Delay, which of the following is true?

- a. The Resistance closest to the load has the highest effect on the delay
- b. The Capacitance closest to the load has the highest effect on the delay
- c. The Resistance closest to the source has the highest effect on the delay
- d. The Capacitance closest to the source has the highest effect on the delay

20. For the figure – 4 shown below, what is the total delay in terms of  $T$ .  $T$  is defined as the delay of a parasitic-free fanout-of-1 inverter? Hint:  $T = 3RC$

- a.  $2T$
- b.  $3T$
- c.  $4T$
- ☒ d.  $5T$

 


Figure – 4 Fanout-of-4 inverter

$\text{fanout component} = 4T$

21. When transistors switch, both nMOS and pMOS networks may be momentarily ON at the same time, leading to a blip of current called short-circuit current

22. Consider a 4 input NAND gate that is sized to provide the same current as a unit inverter. What is the value of  $k$  (width) for the PMOS?

- a.  $k = 1$
- ☒ b.  $k = 2$
- c.  $k = 4$
- d.  $k = 8$

$K_p =$

23. For the NAND gate in problem # 22, what is the value of  $k$  (width of the NMOS) for the NMOS?

- a.  $k = 1$
- b.  $k = 2$
- ☒ c.  $k = 4$
- d.  $k = 8$

$K_n =$

24. For the NAND gate in problem # 22, what is the value of  $g$  (logical effort)? Hint:  $g$  is defined as  $C_{in}(\text{of the gate}) / C_{in}(\text{of a unit inverter})$   $g = (C_{in-gate} / C_{in-unit-inverter})$

- ☒ a.  $g = 6/3$
- b.  $g = 7/3$
- c.  $g = 8/3$
- d.  $g = 9/3$

25. Consider a 4 input NOR gate that is sized to provide the same current as a unit inverter. What is the value of  $g$  (logical effort)? 9/3